

Measuring Inductance

JQI Schine Lab

April 18, 2025

1 Introduction

This report details the procedure and results from an experimental investigation to measure the inductance of a coil constructed from 10 AWG copper wire with approximately 120 turns. Multiple measurement methodologies were employed to compare their accuracy and reliability. The primary aim was to determine the most effective technique for accurately measuring inductance while identifying potential sources of measurement error.

2 Measurements

The inductance of the coil was measured using four different scenarios. Table 1 summarizes the results obtained through these different methodologies. A single measurement of the DC resistance yielded a value of $0.29\,\Omega$.

Table 1: Inductance Measurements Using Different Methodologies

Scenario	Method	Measured Inductance
Scenario 0	Oscilloscope pulse decay measurement	3.80 mH
Scenario 1	RLC circuit with resonance peak analysis	2.85 mH
Scenario 2	LC circuit with resonance peak analysis	4.33 mH
Scenario 3	LC circuit with impedance slope method	4.83 mH

3 Brief Overview

A Bode Plot 100 analyzer was utilized to conduct impedance measurements of both RLC and LC circuit configurations to determine the inductance of the coil. The measurements were performed with three different configurations: with a $1\,\mu\text{F}$ capacitor (C1), with a $100\,\text{nF}$ capacitor (C2), and without any capacitor. Although the Bode plotter features three channels, only the output channel was employed for this experiment, while channels 1 and 2 remained unused.

Figure 1: Circuit Diagram for RLC Configuration


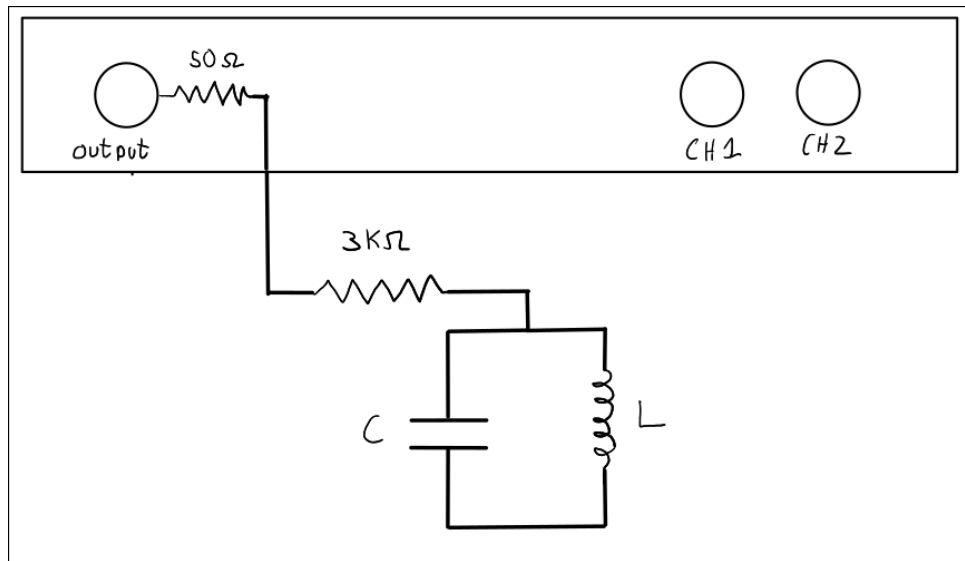



Figure 2: Circuit Diagram for LC Configuration

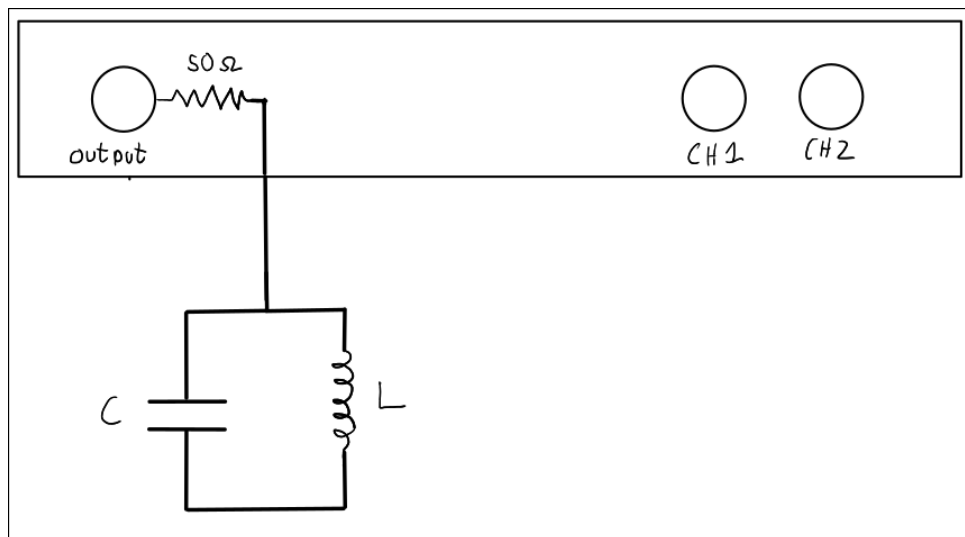

Since the Bode plotter software refused to connect to my Windows system, I opted to use a Linux environment. An SCPI (Standard Commands for Programmable Instruments) server was used to communicate with the Bode Plot 100 analyzer. Please refer to the automation section in <https://www.omicron-lab.com/downloads/bode-analyzer-suite> for more details. While the windows software provides a graphical application, the automated data collection enabled precise frequency sweeps and consistent measurement settings across all test configurations.


4 Initial Planning

Figure 3: Hand-Written Experimental Notes and Planning

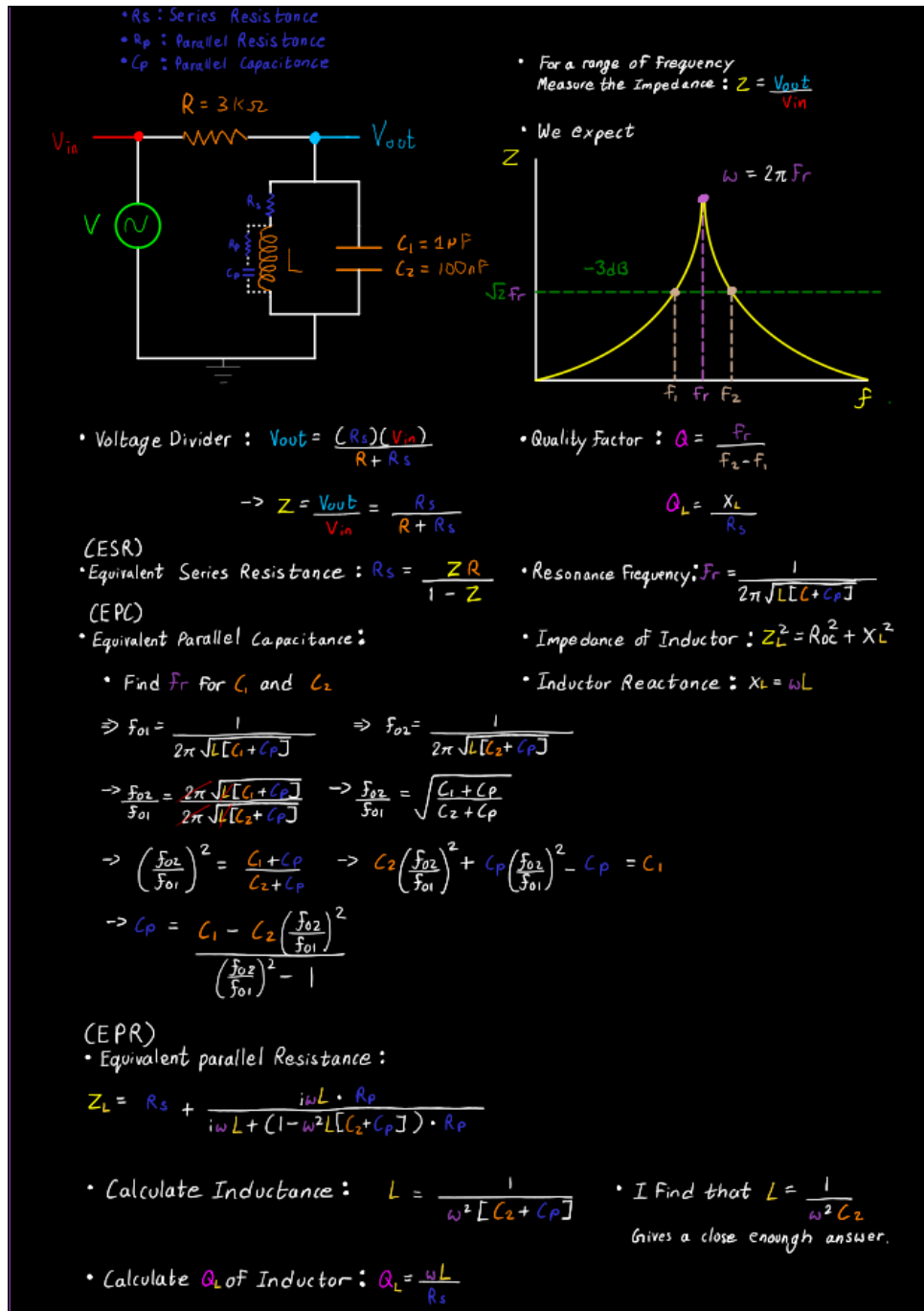

The initial experimental approach utilized an RLC circuit with a $3\text{ k}\Omega$ resistor to measure the inductance of the coil. The impedance characteristics were measured across a frequency range from 10 Hz to 1000 kHz.

Figure 4: Impedance vs. Frequency Plot for RLC Circuit (Log-Log Scale)

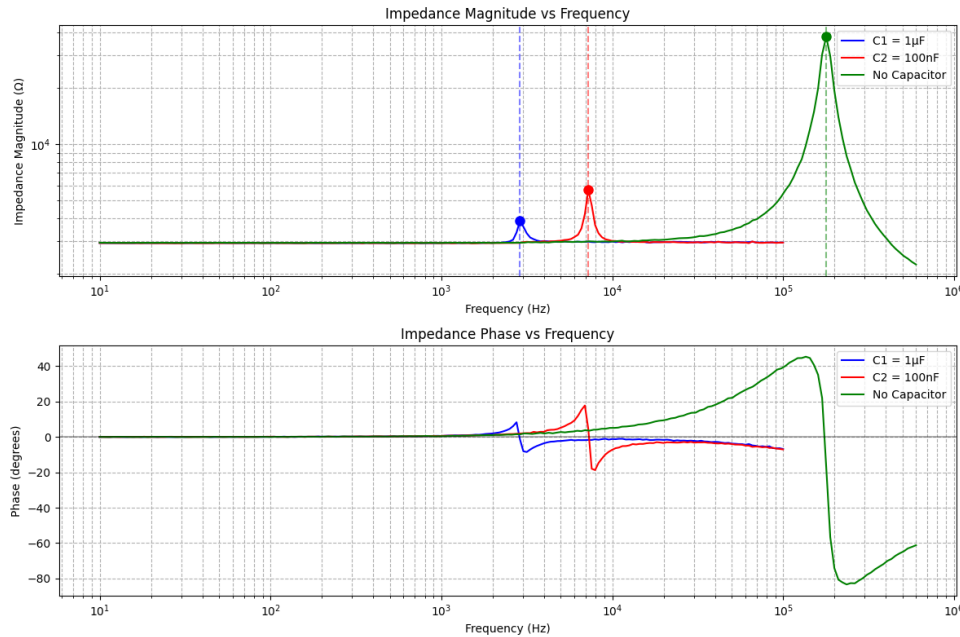


Analysis of the RLC circuit data revealed that the resistive component significantly damped the system's energy, obscuring the expected linear slope in the impedance versus frequency plot that is characteristic of inductive components. Instead, the resonance peaks observed in the frequency response were used to calculate the inductance as detailed in the hand-written notes (Figure 3).

However, it became apparent that the Bode Plotter was measuring the impedance of the entire RLC circuit, not just the inductor. This realization indicated that the calculation methodology outlined in the hand-written notes would be applied incorrectly in this scenario, as it assumes that the impedance-frequency relationship is solely attributed to the inductive component. This discovery prompted a shift to an LC circuit configuration for subsequent measurements.

5 Slope Method

Figure 5: Impedance vs. Frequency Plot for LC Circuit (Log-Log Scale)

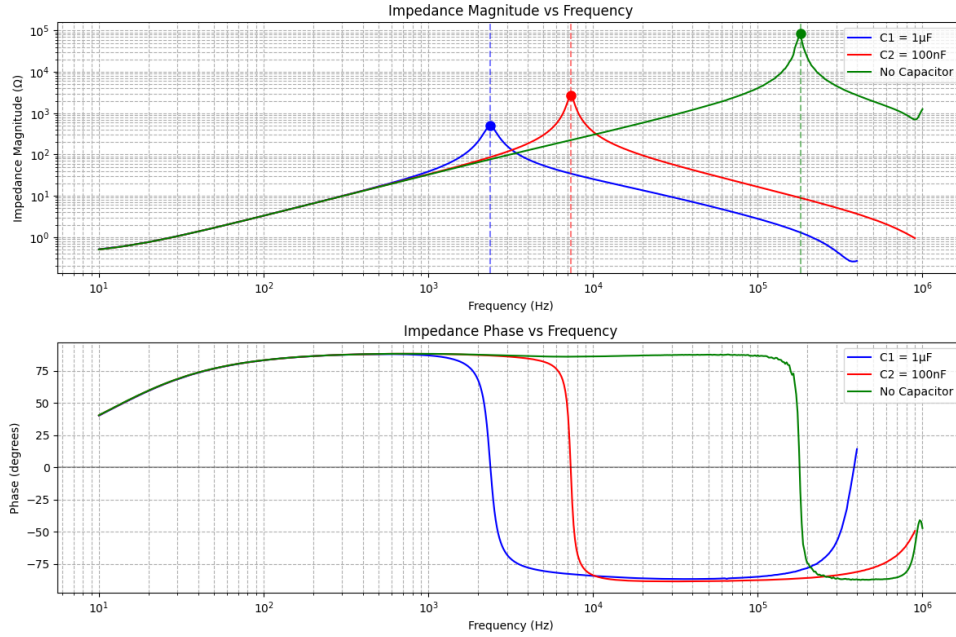

The LC circuit configuration provided clearer measurement data, with all three test configurations (C1, C2, and no capacitor) exhibiting the expected linear slope in the log-log plot of impedance versus frequency. This linear relationship in the logarithmic domain confirms the dominant inductive behavior in the frequency range of interest.

For the inductance calculation, the impedance data from the "no capacitor" configuration was used, as this represents the purest measurement of the inductor's characteristics without the influence of capacitive elements. The slope of this line corresponds directly to the inductor's impedance relationship:

$$Z_L = j\omega L = j2\pi fL \quad (1)$$

Where the magnitude of impedance increases linearly with frequency:

$$|Z_L| = 2\pi fL \quad (2)$$

Thus, the inductance can be calculated from the slope of the impedance versus frequency plot:

$$L = \frac{\text{slope}}{2\pi} \quad (3)$$

This calculation yielded an inductance value of 4.83 mH, which is considered the most accurate measurement from this experimental investigation.

6 Rough Analysis

A theoretical estimation of the inductance can be calculated using the physical dimensions of the coil:

- Relative permeability (μ_r) = 1 (air core)
- Number of turns (N) = 120
- Outer diameter = 0.2 m
- Inner diameter = 0.14 m
- Depth = 0.04 m

For a coil with these dimensions, the theoretical inductance can be calculated using the formula for a toroidal coil with rectangular cross-section:

$$L = \frac{\mu_0 \mu_r N^2 A}{l} \quad (4)$$

Where:

- μ_0 is the permeability of free space $4\pi \times 10^{-7}$
- A is the cross-sectional area of the coil winding
- l is the mean path length of the magnetic flux

Calculating these parameters:

$$\text{Mean diameter} = \frac{0.2 + 0.14}{2} = 0.17 \text{ m} \quad (5)$$

$$\text{Cross-sectional area} = \frac{0.2 - 0.14}{2} \times 0.04 = 0.0012 \text{ m}^2 \quad (6)$$

$$\text{Mean path length} = \pi \times 0.17 = 0.534 \text{ m} \quad (7)$$

Substituting these values:

$$L = \frac{4\pi \times 10^{-7} \times 1 \times 120^2 \times 0.0012}{0.534} \quad (8)$$

$$= \frac{4\pi \times 10^{-7} \times 14400 \times 0.0012}{0.534} \quad (9)$$

$$= \frac{4\pi \times 10^{-7} \times 17.28}{0.534} \quad (10)$$

$$\approx 4.07 \text{ mH} \quad (11)$$

Comparing this theoretical value with our experimental measurements:

- Scenario 0 (Oscilloscope): 3.80 mH (approximately 6.6% below theory)
- Scenario 1 (RLC circuit): 2.85 mH (approximately 30.0% below theory)
- Scenario 2 (LC resonance): 4.33 mH (approximately 6.4% above theory)
- Scenario 3 (LC slope): 4.83 mH (approximately 18.7% above theory)

The measurements from Scenarios 0 and 2 most closely align with the theoretical calculation, with deviations of less than 7%. The significant deviation in Scenario 1 (RLC circuit) may confirm the earlier observation that the resistor component affects the measurement.

7 Code

The following code was implemented in a Jupyter notebook for automated data collection and analysis:

7.1 Block 1: SCPI Server Setup

```

1 # Block 1: SCPI Server Setup
2 import pyvisa
3 import time
4 import matplotlib.pyplot as plt
5 import numpy as np
6 from scipy.optimize import curve_fit
7
8 # *** TO DO: adapt IP address and SCPI port according to your needs ***
9 SCPI_server_IP = 'Server IP given by SCPI server'
10 SCPI_Port = '5025'
11 SCPI_timeout = 20000 # milliseconds
12 VISA_resource_name = 'TCPIP::' + SCPI_server_IP + '::' + SCPI_Port + '::SOCKET'
13
14 # Measurement configuration
15 Start_frequency = '10Hz'
16 Stop_frequency = '1000KHz'
17 Number_of_measurement_points = 601 # the minimum amount of measurement
    points is 2!
18 Sweep_type = 'LOG'
19 Receiver_bandwidth = '300Hz'
20
21 def perform_measurement():
22     start_time = time.time()
23     print(
24         'Trying to connect to VISA resource: ' + VISA_resource_name +
25         '. Be sure that IP address and port number are correct!')
26     visaSession = pyvisa.ResourceManager().open_resource(
27         VISA_resource_name)
28     visaSession.timeout = SCPI_timeout
29     visaSession.read_termination = '\n'
30     print('SCPI client connected to SCPI server: ' + visaSession.query("*IDN?"))
31
32     lockOk = visaSession.query(":SYST:LOCK:REQ?")
33     if lockOk != "1":
34         print("Locking was not successful, exiting!")
35         return None, None, None
36     else:
37         print("Locking was successful!")
38
39     try:
40         ### Here comes the measurement configuration data for
41         measurement sweep
42         visaSession.write(':SENS:FREQ:STAR ' + Start_frequency)
43         visaSession.write(':SENS:FREQ:STOP ' + str(Stop_frequency))
44         visaSession.write(':SENS:SWE:POIN ' + str(
45             Number_of_measurement_points))
46         visaSession.write(':SENS:SWE:TYPE ' + Sweep_type)
47         visaSession.write(':SENS:BAND ' + Receiver_bandwidth)

```

```

45     # configuring 'one-port' impedance measurement
46     visaSession.write(':CALC:PAR:DEF Z')
47     # linear magnitude in Ohms + phase(deg)
48     visaSession.write(":CALC:FORM SLIN")
49
50
51     # Intializes trigger system to use BUS as source
52     visaSession.write(':TRIG:SOUR BUS')
53     # Sets the trigger in continous mode.
54     visaSession.write(':INIT:CONT ON')
55     visaSession.write(':TRIG:SING')
56
57     # This command waits for all pending operations to finish
58     visaSession.query('*OPC?')
59
60     # Query the measurement results
61     allResults = visaSession.query(":CALC:DATA:SDAT?")
62     frequencyValues = visaSession.query(":SENS:FREQ:DATA?")
63
64     # Magnitude and phase from the results
65     allResults_list_raw = list(map(float, allResults.split(",")))
66     magnitude_raw = allResults_list_raw[0:
Number_of_measurement_points]
67     phase_raw = allResults_list_raw[Number_of_measurement_points:len
(allResults_list_raw)]
68
69     # Same procedure with frequency raw data to list and eventually
to array
70     freq_list_raw = list(map(float, frequencyValues.split(",")))
71
72     # Printing just the first results of the measurement cycle as
example
73     print("Frequency: " + str(freq_list_raw[0]) + " Hz;" + "\
tMagnitude: "
74           + str(magnitude_raw[0])
75           + "    ;" + "\tPhase: " + str(phase_raw[0]) + "    ")
76
77     except Exception as e:
78         print(f"An error occurred: {e}")
79         return None, None, None
80
81     finally:
82         # Release the device
83         relOK = visaSession.query(':SYSTEM:LOCK:RElease?')
84         visaSession.query('*OPC?')
85         if relOK != "1":
86             print("Releasing was not successful, check the availability
of the device!")
87         else:
88             print("Releasing was successful!")
89
90     visaSession.close()
91     print("---Measurement time: %s seconds ---" % (time.time() -
start_time))
92
93     return freq_list_raw, magnitude_raw, phase_raw

```

Listing 1: SCPI Server Setup and Connection

7.2 Block 2: First Measurement with $C1 = 1F$

```

1 # Block 2: First Measurement with C1 = 1 F
2 print("Running measurement with C1 = 1 F ")
3 freq1, mag1, phase1 = perform_measurement()
4 #save to csv file
5 np.savetxt("1uF.csv", np.column_stack((freq1, mag1, phase1)), delimiter=
    ",", header="Frequency, Magnitude, Phase", comments='')

```

Listing 2: First Measurement with C1

7.3 Block 3: Second Measurement with $C2 = 100nF$

```

1 # Block 3: Second Measurement with C2 = 100nF
2 print("\nRunning measurement with C2 = 100nF")
3 freq2, mag2, phase2 = perform_measurement()
4 # save to csv file
5 np.savetxt("100nF.csv", np.column_stack((freq2, mag2, phase2)),
    delimiter=",", header="Frequency, Magnitude, Phase", comments='')

```

Listing 3: Second Measurement with C2

7.4 Block 4: Third Measurement with No Capacitor

```

1 # Block 3.1: Third Measurement with no capacitor
2 print("\nRunning measurement with no capacitor")
3 freq3, mag3, phase3 = perform_measurement()
4 #Save to csv file
5 np.savetxt("NoCap.csv", np.column_stack((freq3, mag3, phase3)),
    delimiter=",", header="Frequency, Magnitude, Phase", comments='')
6 plt.figure()
7 plt.loglog(freq3, mag3)
8 plt.show()

```

Listing 4: Third Measurement with No Capacitor

7.5 Block 5: Analysis and Plotting

```

1 # Block 4: Analysis and Plotting
2 import numpy as np
3 import matplotlib.pyplot as plt
4
5 fre1 = np.loadtxt("1uF.csv", delimiter=",", skiprows=1)
6 fre2 = np.loadtxt("100nF.csv", delimiter=",", skiprows=1)
7 fre3 = np.loadtxt("NoCap.csv", delimiter=",", skiprows=1)
8 freq1 = [n for n in fre1[:,0]]
9 mag1 = [n for n in fre1[:,1]]
10 phase1 = [n for n in fre1[:,2]]
11 freq2 = [n for n in fre2[:,0]]
12 mag2 = [n for n in fre2[:,1]]
13 phase2 = [n for n in fre2[:,2]]
14 freq3 = [n for n in fre3[:,0]]
15 mag3 = [n for n in fre3[:,1]]
16 phase3 = [n for n in fre3[:,2]]
17

```

```

18 # Find resonant frequencies by finding MAXIMUM impedance magnitude (for
    # parallel resonance)
19     # Find maximum impedance (peak in the bode plot)
20 max_idx1 = mag1.index(max(mag1))
21 fr1 = freq1[max_idx1]
22 z_max1 = mag1[max_idx1]
23 print(f"Resonant frequency (C1): {fr1:.2f} Hz, Maximum impedance: {
    z_max1:.2f} ")
24
25 # Find maximum impedance (peak in the bode plot)
26 max_idx2 = mag2.index(max(mag2))
27 fr2 = freq2[max_idx2]
28 z_max2 = mag2[max_idx2]
29 print(f"Resonant frequency (C2): {fr2:.2f} Hz, Maximum impedance: {
    z_max2:.2f} ")
30
31 # Find maximum impedance (peak in the bode plot)
32 max_idx3 = mag3.index(max(mag3))
33 fr3 = freq3[max_idx3]
34 z_max3 = mag3[max_idx3]
35 print(f"Resonant frequency (No Capacitor): {fr3:.2f} Hz, Maximum
    impedance: {z_max3:.2f} ")
36
37
38 '''
39 Invalid way of calculating the EPC and L
40
41 # Calculate component values if resonant frequencies were found
42 if fr1 and fr2:
43     # Given values
44     C1 = 1e-6 # 1 F
45     C2 = 100e-9 # 100nF
46
47     # Calculate inductance using equation
48     #  $fr = 1/(2 \sqrt{L(C+C_p)})$ 
49     # Two measurements with different capacitors allow us to solve for L
50
51     # Using the formula derived
52     #  $(fr2/fr1)^2 = (C1+C_p)/(C2+C_p)$ 
53     # Solve for Cp (Equivalent Parallel Capacitance)
54     ratio_sq = (fr2/fr1)**2
55     Cp = (C1 - ratio_sq * C2) / (ratio_sq - 1)
56     print(f"Equivalent Parallel Capacitance (Cp): {Cp*1e9:.2f} nF")
57
58     # Calculate inductance using fr1 and total capacitance (C1 + Cp)
59     L = 1 / ((2 * np.pi * fr1)**2 * (C1 + Cp))
60     print(f"Inductance (L): {L*1e3:.2f} mH")
61
62     # Calculate Slope of the plot at 100Hz to 300Hz by fitting to a line
63
64
65 if fr3:
66     L_wc = 1 / (2 * np.pi * fr3)
67     print(f"Inductance without cap (L_wc): {L*1e3:.2f} mH")
68
69     # using  $fr = 1/(2 \sqrt{LC})$  where  $C_p = C$ 
70     Cp_wc = 1 / (4 * (np.pi**2) * (fr3**2) * L_wc)
71     print(f"Parasitic Capacitance (Cp_wc): {Cp_wc*1e9:.2f} nF")

```

```

72 '''
73 # Use the slope of the plot to calculate the inductance
74 def calculate_inductance_from_slope(freq, mag, freq_start, freq_end):
75     # Find indices for the frequency range
76     indices = [i for i, f in enumerate(freq) if freq_start <= f <=
freq_end]
77
78     # Extract the relevant portions of the data
79     freq_range = [freq[i] for i in indices]
80     mag_range = [mag[i] for i in indices]
81
82     # Fit a line to the data
83     coeffs = np.polyfit(freq_range, mag_range, 1)
84     slope = coeffs[0]
85     intercept = coeffs[1]
86
87     # For an inductor,  $|Z| = L \cdot 2\pi f$ 
88     #  $L = \text{slope} / (2\pi)$ 
89     L = slope / (2 * np.pi)
90
91     return L, slope, intercept, freq_range, mag_range
92
93 # Set frequency range for analysis
94 freq_start = 10**2 # Hz
95 freq_end = 10**4 # Hz
96
97 # Choose which dataset to use ('C1', 'C2', or 'noCapacitor')
98 dataset = 'noCapacitor' # Change this to use different dataset
99
100 # Calculate inductance based on chosen dataset
101 if dataset == 'C1':
102     L, slope, intercept, freq_range, mag_range =
calculate_inductance_from_slope(
103         freq1, mag1, freq_start, freq_end)
104     label = "C1 = 1 F "
105 elif dataset == 'C2':
106     L, slope, intercept, freq_range, mag_range =
calculate_inductance_from_slope(
107         freq2, mag2, freq_start, freq_end)
108     label = "C2 = 100nF"
109 elif dataset == 'noCapacitor':
110     L, slope, intercept, freq_range, mag_range =
calculate_inductance_from_slope(
111         freq3, mag3, freq_start, freq_end)
112     label = "No Capacitor"
113
114 # Print results
115 if L is not None:
116     print(f"\nInductance calculation using {label} (slope between {
freq_start}-{freq_end} Hz):")
117     print(f"    Linear fit:  $|Z| = \text{slope} \cdot f + \text{intercept}$ ")
118     print(f"    Slope: {slope} /Hz")
119     print(f"    Inductance: {L*1e3:.2f} mH")
120 else:
121     print(f"Could not calculate inductance for {label} in range {
freq_start}-{freq_end} Hz")
122
123 #  $w = 2\pi f$  measured DC Resistance = mdr # Ohm

```

```

124 mdr = 0.29
125 w1 = 2 * np.pi * fr1
126 w2 = 2 * np.pi * fr2
127 w3 = 2 * np.pi * fr3
128 Q1 = w1*L/mdr
129 print("Q factor with C1 = 1 F : ", Q1)
130 Q2 = w2*L/mdr
131 print("Q factor with C2 = 100nF: ", Q2)
132 Q3 = w3*L/mdr
133 print("Q factor with no capacitor: ", Q3)
134
135 # Plot the results
136 plt.figure(figsize=(12, 8))
137
138 # Plot 1: Magnitude vs Frequency
139 plt.subplot(2, 1, 1)
140 if freq1 and mag1:
141     plt.loglog(freq1, mag1, 'b-', label='C1 = 1 F ')
142     plt.axvline(x=fr1, color='b', linestyle='--', alpha=0.5)
143     plt.plot(fr1, z_max1, 'bo', markersize=8)
144
145
146 if freq2 and mag2:
147     plt.loglog(freq2, mag2, 'r-', label='C2 = 100nF')
148     plt.axvline(x=fr2, color='r', linestyle='--', alpha=0.5)
149     plt.plot(fr2, z_max2, 'ro', markersize=8)
150
151 if freq3 and mag3:
152     plt.loglog(freq3, mag3, 'g-', label='No Capacitor')
153     plt.axvline(x=fr3, color='g', linestyle='--', alpha=0.5)
154     plt.plot(fr3, z_max3, 'go', markersize=8)
155
156
157 plt.grid(True, which="both", ls="--")
158 plt.xlabel('Frequency (Hz)')
159 plt.ylabel('Impedance Magnitude ( )')
160 plt.title('Impedance Magnitude vs Frequency')
161 plt.legend()
162
163 # Plot 2: Phase vs Frequency
164 plt.subplot(2, 1, 2)
165 if freq1 and phase1:
166     plt.semilogx(freq1, phase1, 'b-', label='C1 = 1 F ')
167 if freq2 and phase2:
168     plt.semilogx(freq2, phase2, 'r-', label='C2 = 100nF')
169 if freq3 and phase3:
170     plt.semilogx(freq3, phase3, 'g-', label='No Capacitor')
171 plt.grid(True, which="both", ls="--")
172 plt.xlabel('Frequency (Hz)')
173 plt.ylabel('Phase (degrees)')
174 plt.title('Impedance Phase vs Frequency')
175 plt.axhline(y=0, color='k', linestyle='--', alpha=0.3)
176 plt.legend()
177 plt.tight_layout()
178 plt.show()

```

Listing 5: Analysis and Plotting